



Consider the RC circuit in that figure the switch is closed at $t = 0$. Before the switch closing, the capacitor C_1 is charged to V_0 volt and the capacitor C_2 is not charged.

a). Assuming $C_1 = C_2 = C$, find the current $i(t)$ for $t \geq 0$

Dari loop $i(t)$ didapat :

$$-V_{C1} + V_R + V_{C2} = 0$$

$$V_R + V_{C2} = V_{C1}$$

$$R \cdot i(t) + \frac{1}{C_2} \int_{-\infty}^t i(t) dt = V_0 - \frac{1}{C_1} \int_0^t i(t) dt$$

$$R \cdot i(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt = V_0 - \frac{1}{C} \int_0^t i(t) dt$$

$$R \cdot i(s) + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{1}{s} \int_{-\infty}^0 i(t) dt \right] = \frac{V_0}{s} - \frac{1}{C} \cdot \frac{I(s)}{s}$$

$$\text{dengan } V_{C2}(0^-) = \frac{1}{C} \int_{-\infty}^{0^-} i(t) dt = 0$$

Kapasitor 2 kosong selama saklar belum close ($t < 0$)

$$R I(s) + \frac{1}{Cs} + I(s) = \frac{V_0}{s} - \frac{1}{Cs} I(s)$$

$$R I(s) = \frac{2}{Cs} I(s) = \frac{V_0}{s}$$

$$\left(R + \frac{2}{Cs} \right) I(s) = \frac{V_0}{s}$$

$$I(s) = \frac{V_0}{s} \cdot \frac{1}{R + 2/Cs} \rightarrow \text{dikali } \frac{s/R}{s/R}$$

$$I(s) = \frac{V_0}{R} \cdot \frac{1}{s + 2/RC}$$

$$I(t) = \frac{V_0}{R} \cdot e^{-2t/RC}$$

b). Find the total energy E dissipated by the resistor and show that E is independent of R is equal to half of the initial energy

Energi rangkaian = $\frac{1}{2} CV^2 \rightarrow$ energi tersebut tidak tergantung oleh R

$$C \text{ pengganti} = C = C_1 + C_2 = 2C$$

V_1 dan V_2 besarnya sama saat rangkaian tertutup yaitu $\frac{V_1}{2}$

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} 2C \left(\frac{V_1}{2} \right)^2$$

$$= C \frac{V_1^2}{4}$$

$$= \frac{1}{4} CV_1^2 \rightarrow V_1 = V_0$$

$$= \frac{1}{4} CV_0^2$$

$$\text{Besarnya energi di } C_1 = \frac{1}{2} CV_0^2$$

$$\text{Besarnya energi disipasi} = \frac{1}{4} CV_0^2$$

$$\frac{1}{4} C V_0^2 = n \left[\frac{1}{2} C V_0^2 \right]$$

$$n = \frac{1}{2}$$

besar energi disipasi = $\frac{1}{2}$ energi pada C_1

C. Assume that $R = 0$ and $C_1 = C_2 = C$. Find the current $i(t)$ for $t \geq 0$ and voltage $V_{C_1}(0^+)$ and $V_{C_2}(0^+)$

$$R = 0$$

$$C_1 = C_2 = C$$

Dari loop didapatkan :

$$-V_C + V_R + V_{C_2} = 0$$

$$V_R + V_{C_2} = V_{C_1}$$

$$V_{C_2} = V_{C_1}$$

$$\frac{1}{C_2} \int_{-\infty}^t i(t) dt = V_0 - \frac{1}{C_1} \int_0^t i(t) dt$$

$$\frac{1}{C} \int_{-\infty}^t i(t) dt = V_0 - \frac{1}{C} \int_0^t i(t) dt$$

$$\frac{1}{C} \left[\frac{I(s)}{s} + \frac{1}{s} \int_{-\infty}^0 i(t) dt \right] = \frac{V_0}{s} - \frac{1}{C} \frac{I(s)}{s}$$

$$\frac{1}{C_s} \cdot I(s) + 0 = \frac{V_0}{s} - \frac{1}{C_s} \cdot I(s)$$

$$\frac{2}{C_s} \cdot I(s) = \frac{V_0}{s}$$

$$I(s) = \frac{V_0}{2} \cdot \frac{C_s}{s}$$

$$I(s) = \frac{V_0}{2} \cdot C$$

$$I(s) \rightarrow i(t)$$

$$1 \rightarrow \delta(t)$$

$$i(t) = \frac{1}{2} V_0 C \delta(t)$$

$$V_C = \frac{1}{C} \int i(t) dt$$

$$C_1 = C_2 = C$$

$$V_{C_1} = V_{C_2} = V_C$$

$$V_C = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{C} \int C \frac{1}{2} V_0 \cdot C \delta(t) dt$$

$$= \frac{1}{C} \cdot \frac{1}{2} \cdot V_0 \cdot C$$

$$V_C = \frac{V_0}{2}$$

$$V_{C_1}(0^+) = \frac{V_0}{2}$$

$$V_{C_2}(0^+) = \frac{V_0}{2}$$